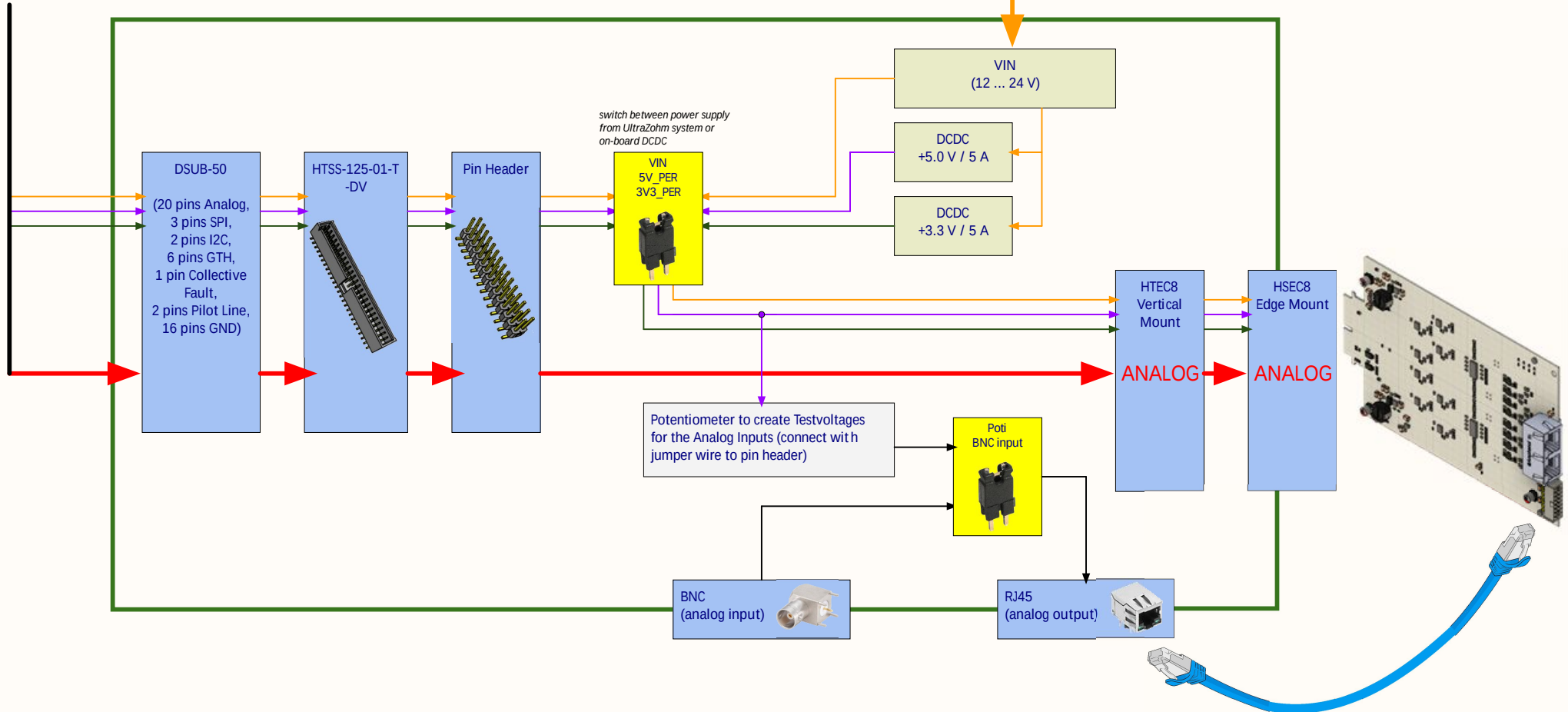




Title UZ_A_Testboard_Block_Diagram.SchDoc

Revision: Rev01

Design Engineer: Andreas Geiger

Project: UZ_A_Testboard.PrjPcb

UltraZohm

www.ultrazohm.com






Date: 07.12.2022

Sheet 1 of 6



HTEC8 Vertical Mount

HSEC8 Edge Mount

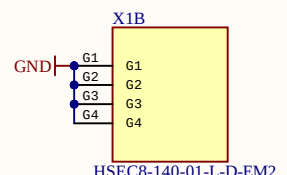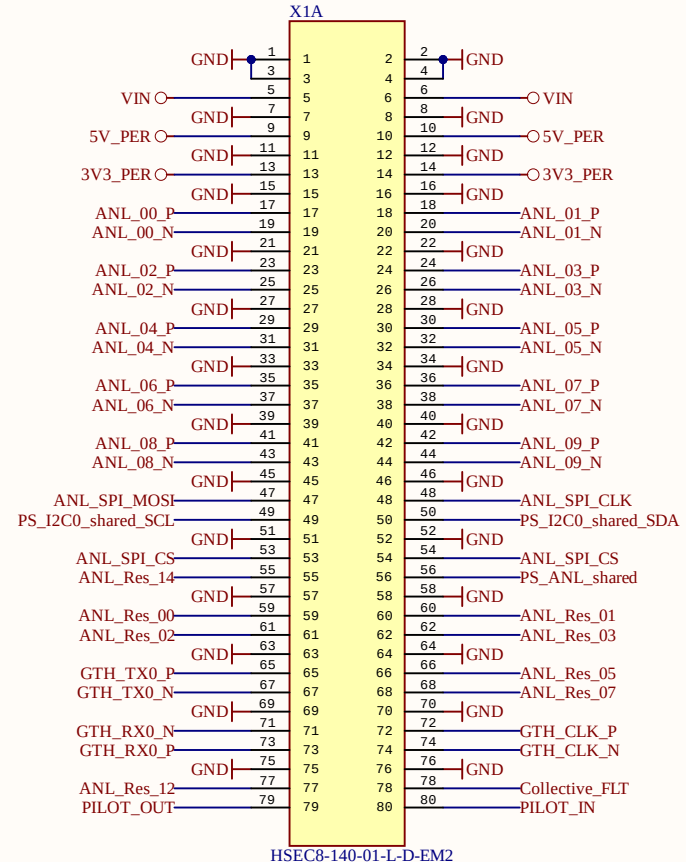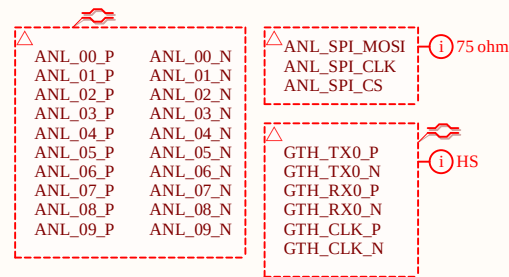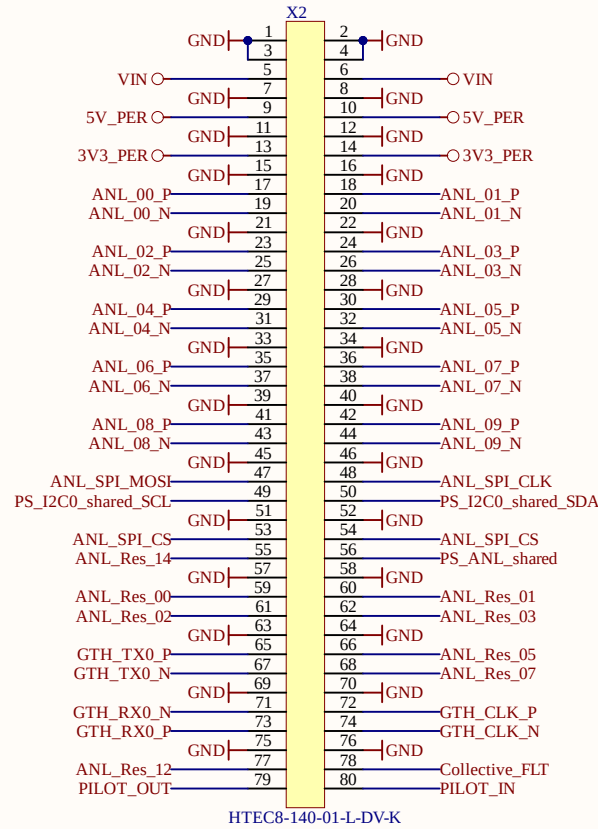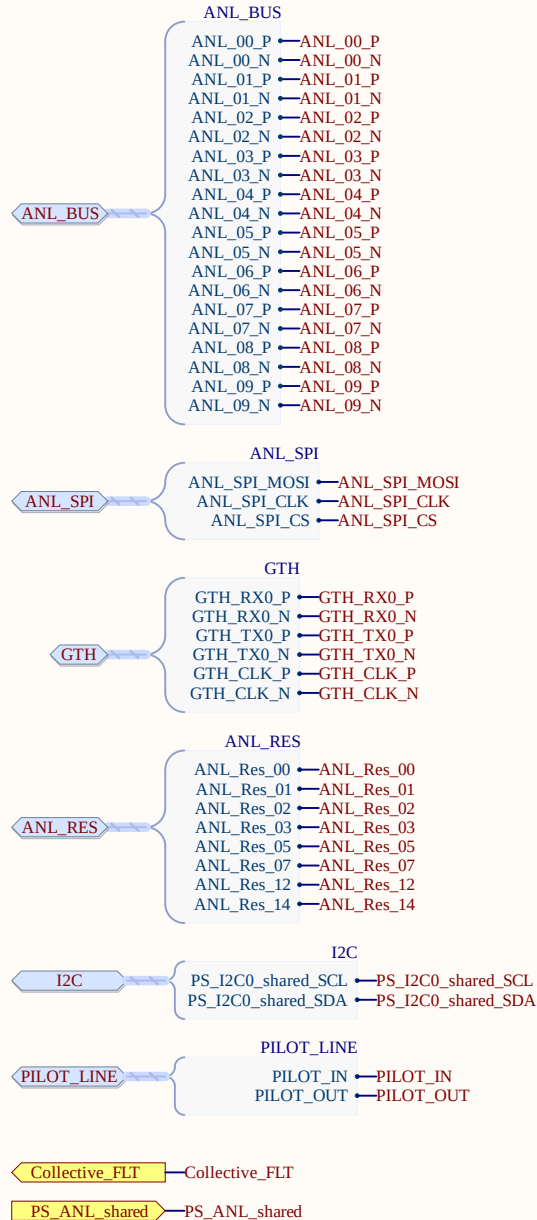

Title Adapter_Card_Connector.SchDoc		UltraZohm www.ultrazohm.com	
Revision: Rev01	Design Engineer: Andreas Geiger		
Project: UZ_A_Testboard.PrjPcb			
		Date: 07.12.2022	Sheet 2 of 6

ANL_BUS

ANL_00_P → ANL_00_P
ANL_00_N → ANL_00_N
ANL_01_P → ANL_01_P
ANL_01_N → ANL_01_N
ANL_02_P → ANL_02_P
ANL_02_N → ANL_02_N
ANL_03_P → ANL_03_P
ANL_03_N → ANL_03_N
ANL_04_P → ANL_04_P
ANL_04_N → ANL_04_N
ANL_05_P → ANL_05_P
ANL_05_N → ANL_05_N
ANL_06_P → ANL_06_P
ANL_06_N → ANL_06_N
ANL_07_P → ANL_07_P
ANL_07_N → ANL_07_N
ANL_08_P → ANL_08_P
ANL_08_N → ANL_08_N
ANL_09_P → ANL_09_P
ANL_09_N → ANL_09_N

ANL_BUS

ANL_SPI

ANL_SPI_MOSI → ANL_SPI_MOSI
ANL_SPI_CLK → ANL_SPI_CLK
ANL_SPI_CS → ANL_SPI_CS

ANL_SPI

GTH

GTH_RX0_P → GTH_RX0_P
GTH_RX0_N → GTH_RX0_N
GTH_TX0_P → GTH_TX0_P
GTH_TX0_N → GTH_TX0_N
GTH_CLK_P → GTH_CLK_P
GTH_CLK_N → GTH_CLK_N

GTH

ANL_RES

ANL_Res_00 → ANL_Res_00
ANL_Res_01 → ANL_Res_01
ANL_Res_02 → ANL_Res_02
ANL_Res_03 → ANL_Res_03
ANL_Res_05 → ANL_Res_05
ANL_Res_07 → ANL_Res_07
ANL_Res_12 → ANL_Res_12
ANL_Res_14 → ANL_Res_14

ANL_RES

I2C

PS_I2C0_shared_SCL → PS_I2C0_shared_SCL
PS_I2C0_shared_SDA → PS_I2C0_shared_SDA

I2C







PILOT_LINE

PILOT_IN → PILOT_IN
PILOT_OUT → PILOT_OUT

PILOT_LINE

Collective_FLT → Collective_FLT

PS_ANL_shared → PS_ANL_shared

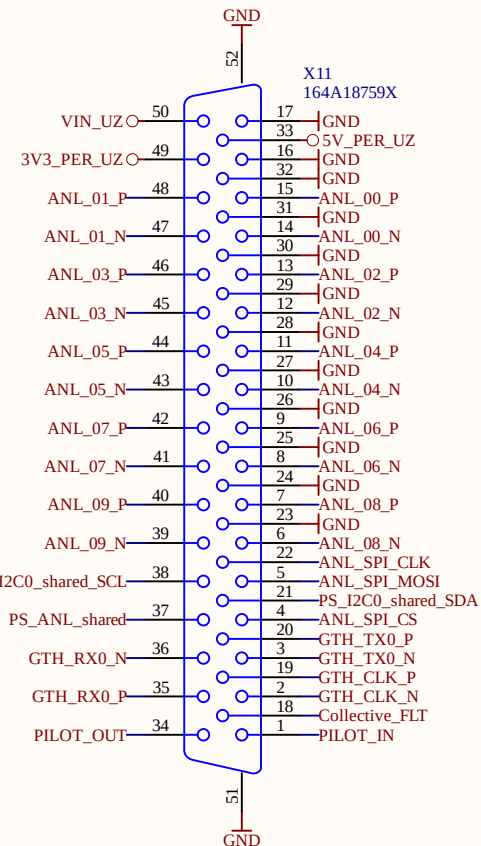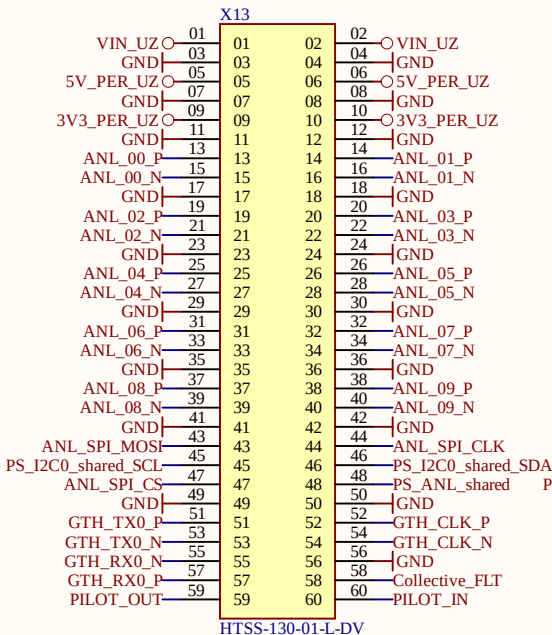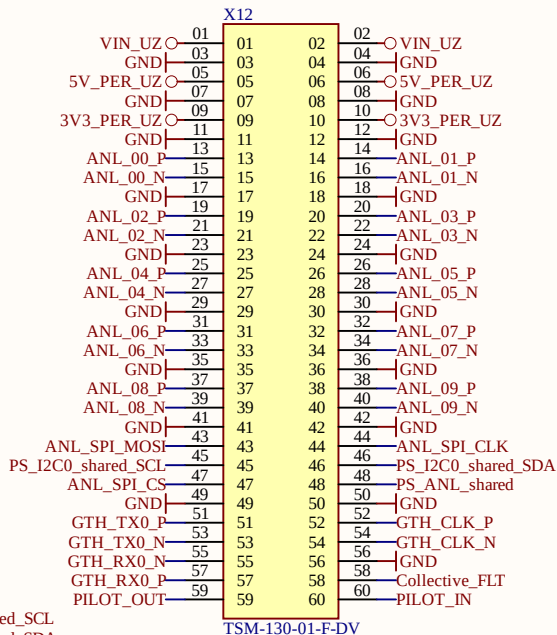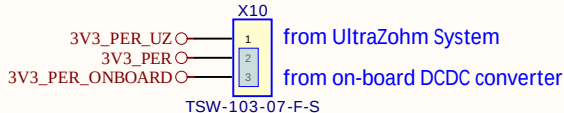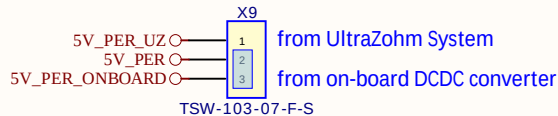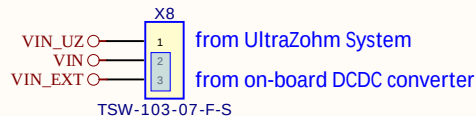

Title Breakout_Connector.SchDoc

Revision: Rev01

Design Engineer: Andreas Geiger

Project: UZ_A_Testboard.PrjPcb





UltraZohm

www.ultrazohm.com


Date: 07.12.2022

Sheet 3 of 6





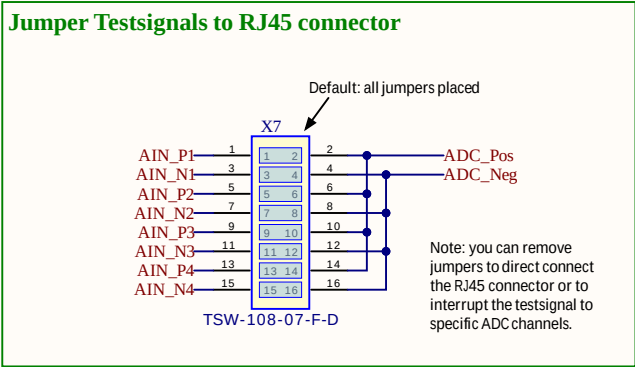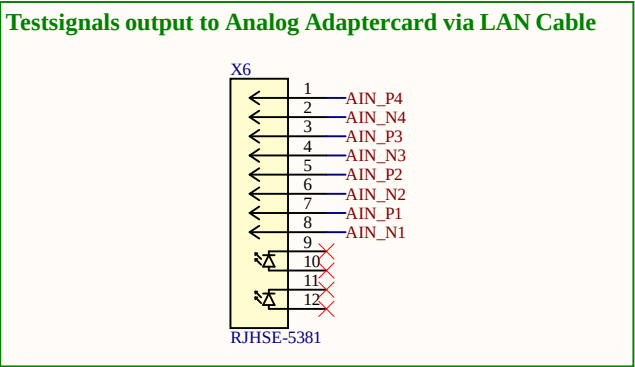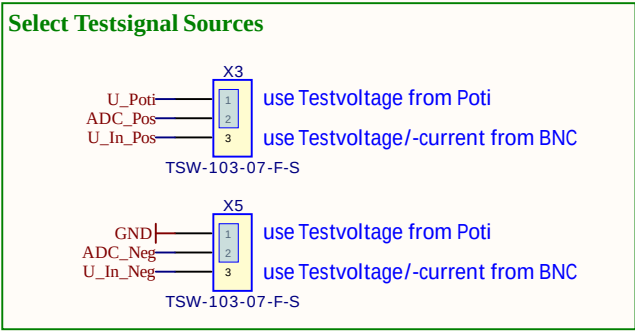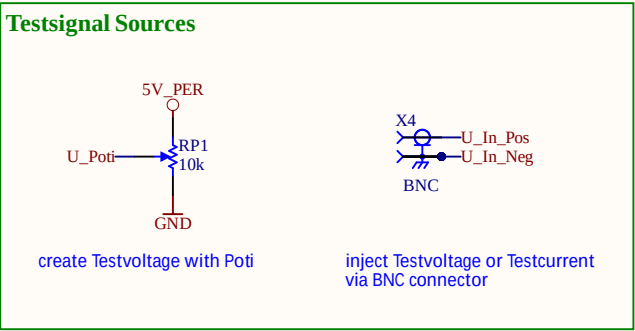

External Laboratory Power Supply

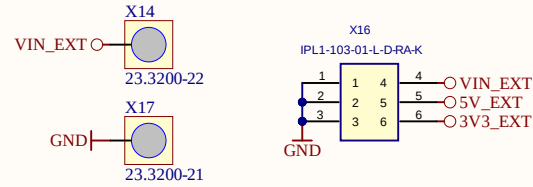


Choose Power Supply Source

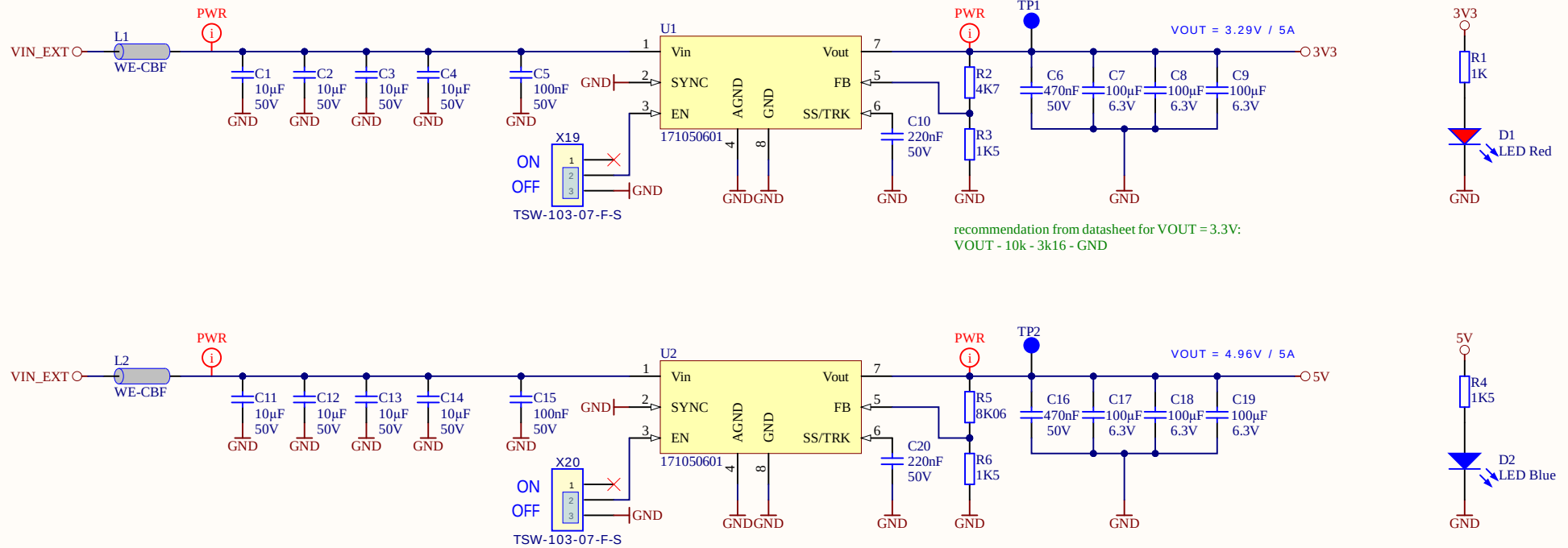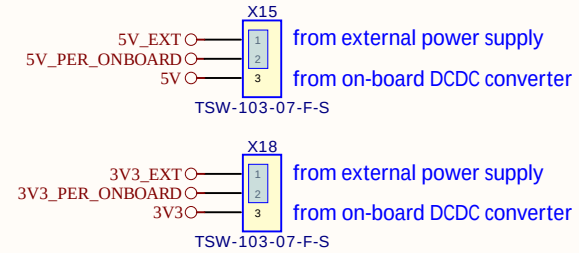


A

A

U_Power_Supply
Power_Supply.SchDoc

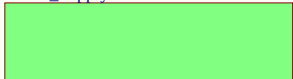

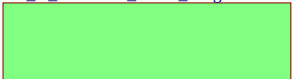U_Block_Diagram
UZ_A_Testboard_Block_Diagram.SchDoc




U_Analog_Testvoltage_Output
Analog_Testvoltage_Output.SchDoc





B

B

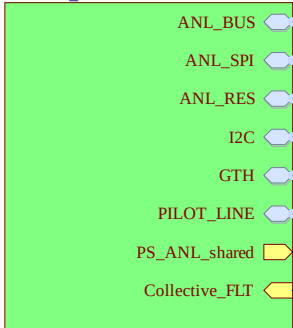U_Breakout_Connector
Breakout_Connector.SchDoc



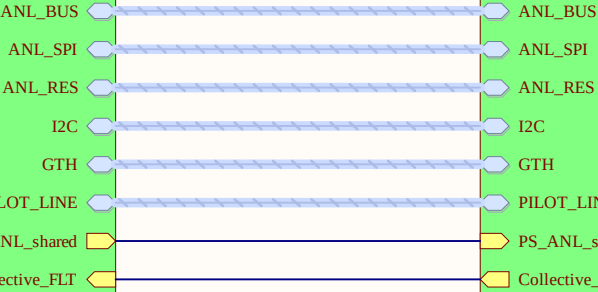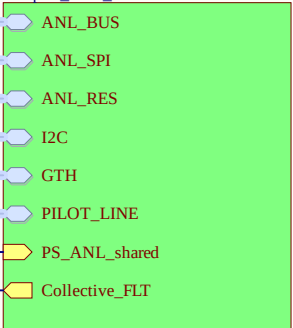U_Adapter_Card_Connector
Adapter_Card_Connector.SchDoc



C

C

LOGO1



UZ Logo

Serial
Serialnumber 6,3 x 6.3mm

D

D

Title Topsheet.SchDoc		UltraZohm www.ultrazohm.com	
Revision: Rev01	Design Engineer: Andreas Geiger		
Project: UZ_A_Testboard.PrjPcb			
		Date: 07.12.2022	
		Sheet 5 of 6	